

0x0E - Pipelining

ENGR 3410: Computer Architecture


Jon Tse

Fall 2020

Today

- Introduction to Pipelining
- Glance at Hazards


CPU Execution Overview

 

- Fetch instruction from memory
- Decode instruction into actions/controls
- Fetch/Decode operands
- Compute result value or status
- Push result(s) to storage
- Determine next instruction

Pipelining

Example: Doing the laundry

 


Ann, Brian, Cathy, & Dave
each have one load of clothes to wash, dry, and fold

Washer takes 30 minutes




Dryer takes 40 minutes

 

“Folder” takes 20 minutes




Sequential Laundry

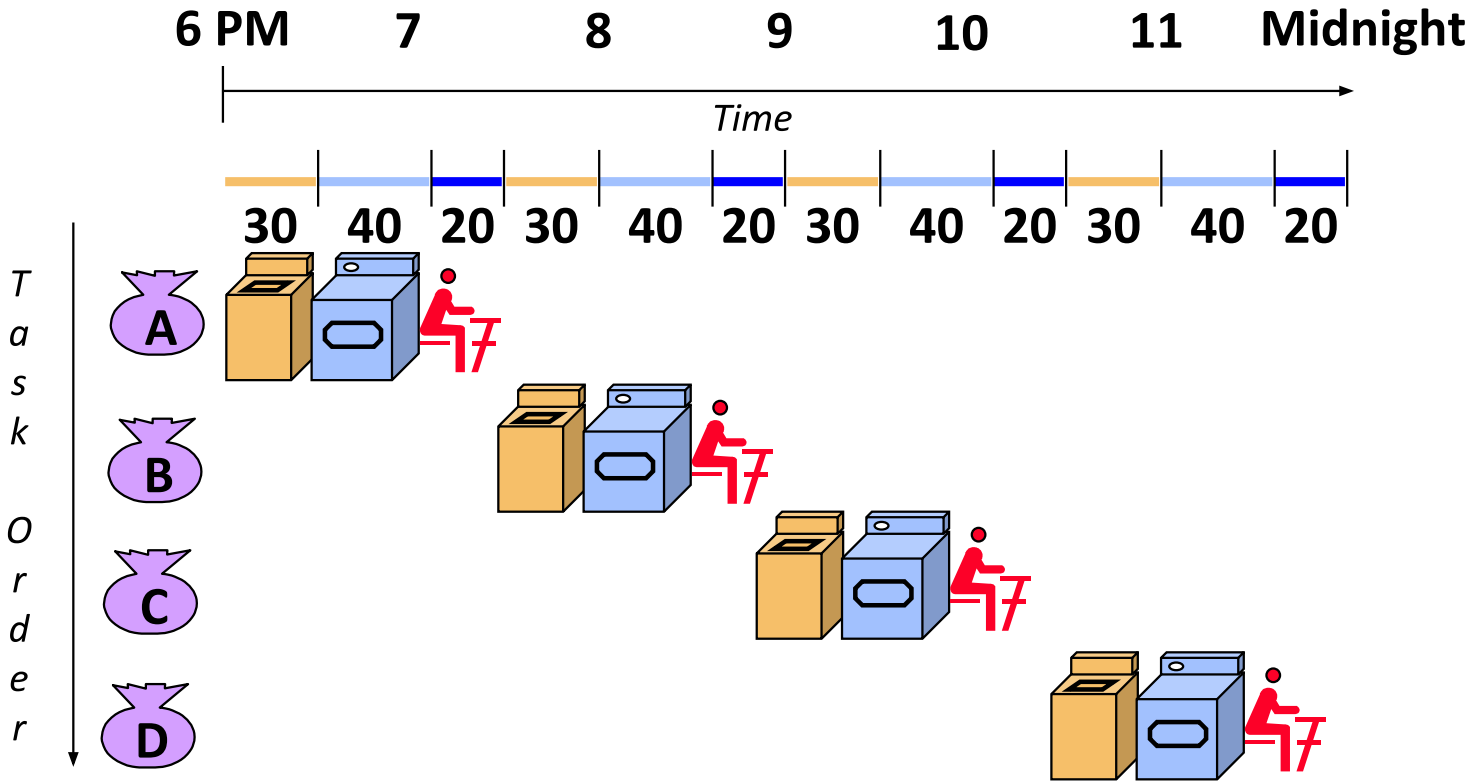

Sequential laundry takes 6 hours for 4 loads


If they learned pipelining, how long would laundry take?

Pipelined Laundry: Start work ASAP

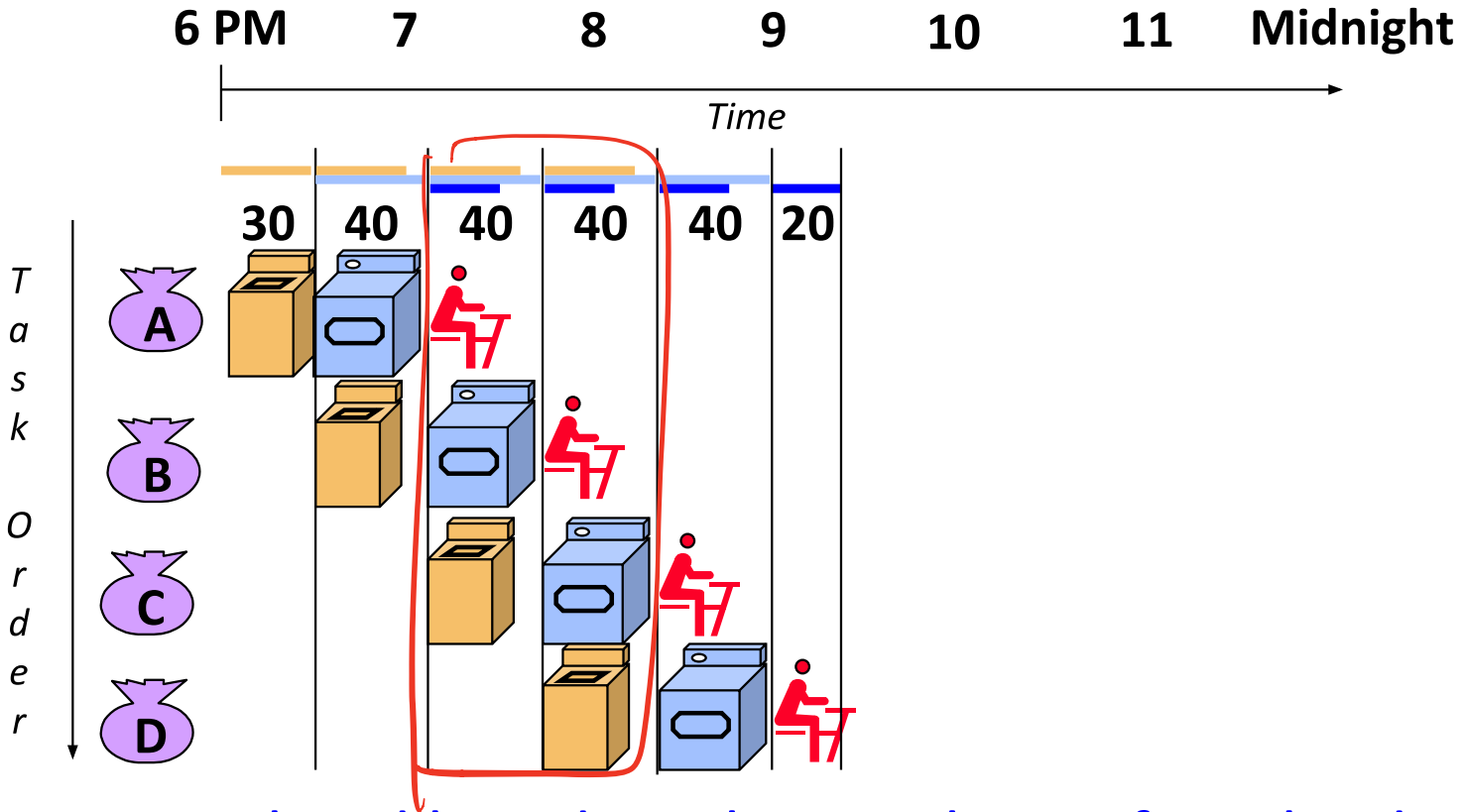


- Pipelined laundry takes 3.5 hours for 4 loads

Pipelining Lessons

 

- Pipelining doesn't help **latency** of single task, it helps **throughput** of entire workload
- Pipeline rate limited by **slowest** pipeline stage
- **Multiple** tasks operating simultaneously using different resources
- Potential speedup = **Number pipe stages**
- Unbalanced lengths of pipe stages reduces speedup
- Time to “**fill**” pipeline and time to “**drain**” it reduces speedup

Pipelined Execution

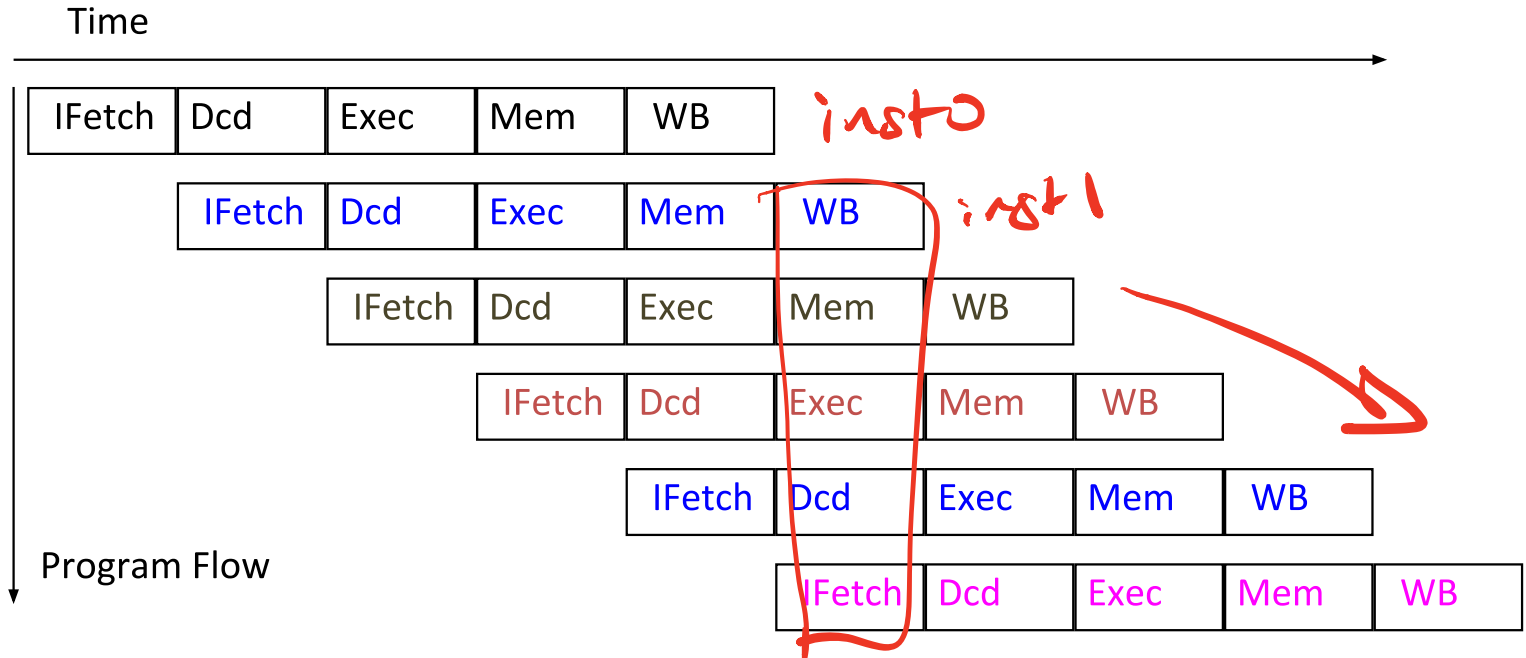

- Ignore fill/drain, ignore latency
- Pipelining maximizes **throughput**

Why Pipeline?

IP ID EX mEm WR
50 ns

Suppose we execute 100 instructions

Single Cycle Machine

5000
-50 ns/cycle x 1 CPI x 100 inst = _____ ns

Ideal pipelined machine

1040
-10 ns/cycle x (1 CPI x 100 inst + 4 cycle drain) = _____ ns


104

Rules of Pipelining

- Divide CPU / Instruction into **stages**
- Each functional unit belongs to one stage
 - Can't reuse e.g. the ALU like a multi-cycle design
 - Reg File R/W ports act as **separate** functional units
 - For now, split memory into instruction & data
- Stage order is the same for all instructions
 - How can you “skip” a stage?
 - This is true for “purely” pipelined processors


Pipelined Datapath

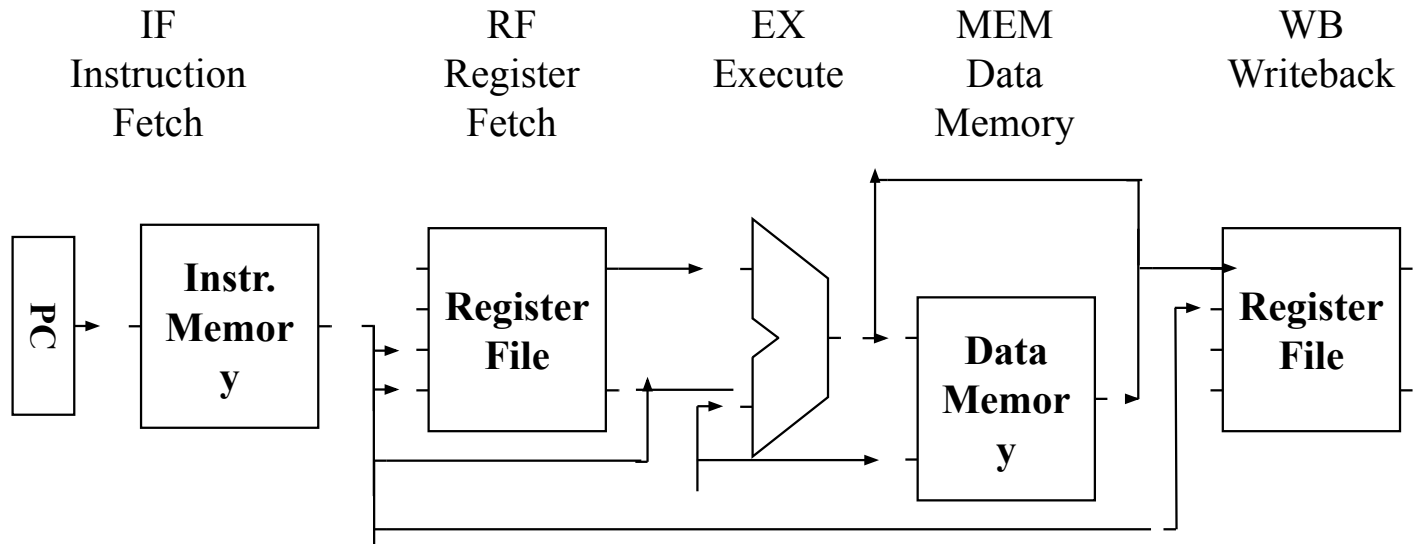- Divide datapath into multiple pipeline stages




Pipelined Datapath

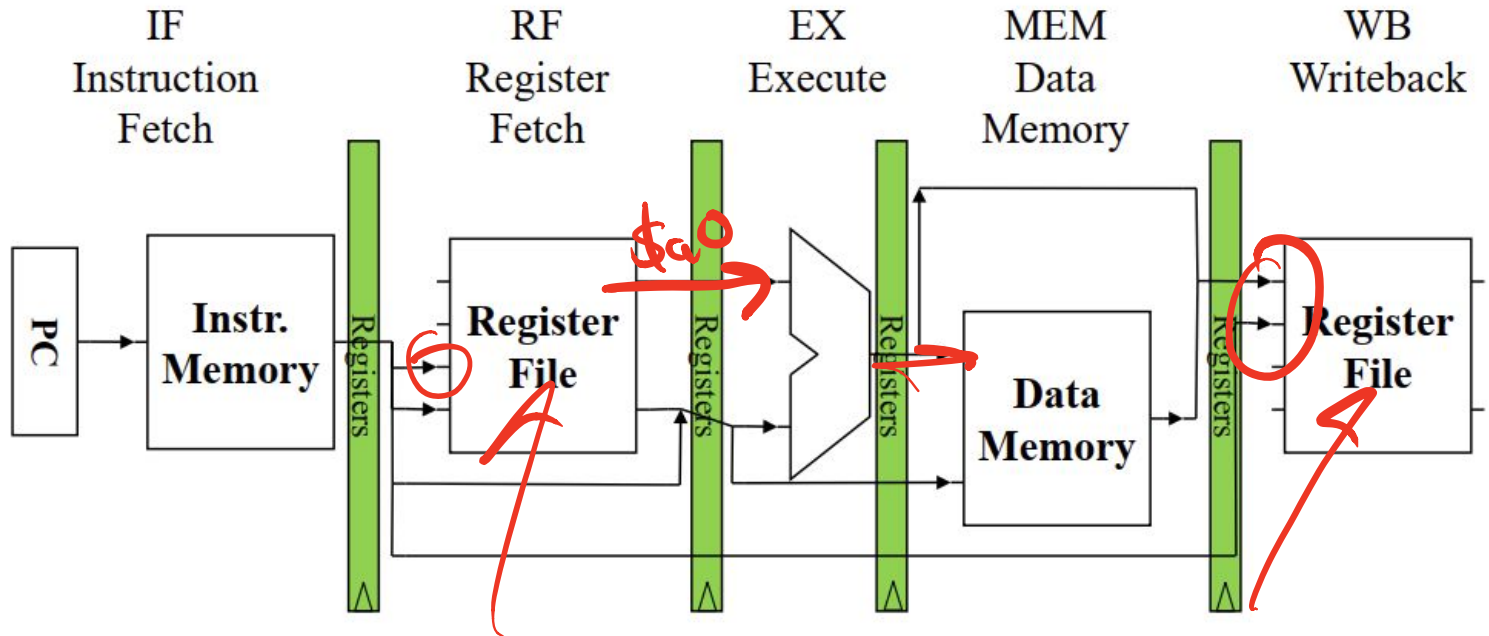- Divide datapath into multiple pipeline stages




Pipelined Control

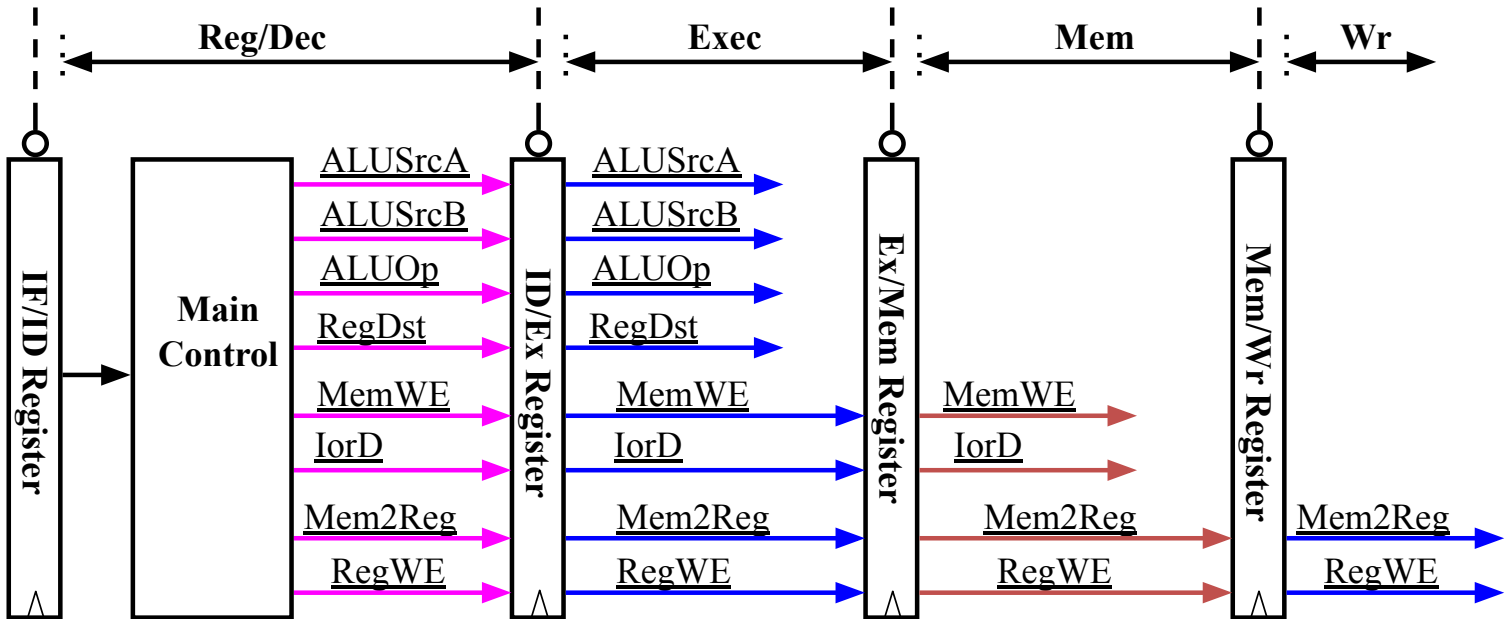- The Main Control generates the control signals during Reg/Dec
 - Control signals for Exec (ALUOp, ALUSrcA, ...) are used 1 cycle later
 - Control signals for Mem (MemWE, IorD, ...) are used 2 cycles later
 - Control signals for Wr (Mem2Reg, RegWE, ...) are used 3 cycles later




Pipelining the Load Instruction

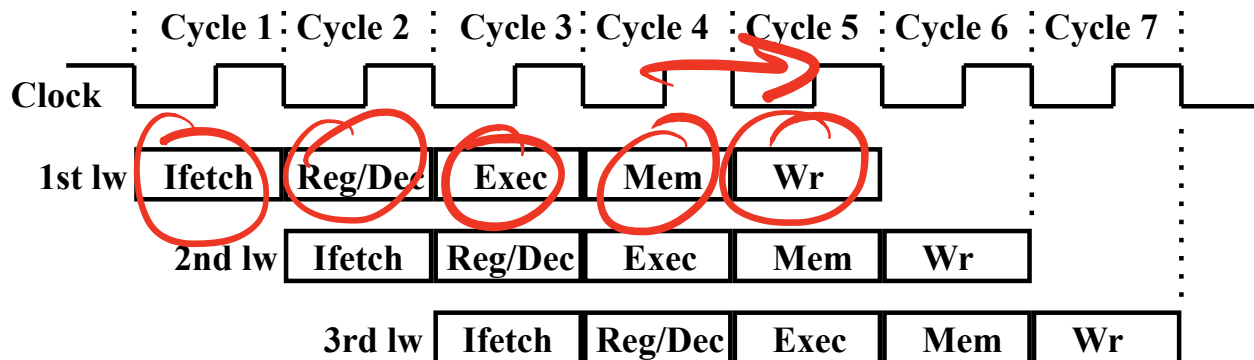- The five independent functional units in the pipeline datapath are:
 - Instruction Memory for the **Ifetch** stage
 - Register File's Read ports (bus A and busB) for the **Reg/Dec** stage
 - ALU for the **Exec** stage
 - Data Memory for the **Mem** stage
 - Register File's Write port (bus W) for the **Wr** stage




The Four Stages of R-type

 - Ifetch: Fetch the instruction from the Instruction Memory
- Reg/Dec: Register Fetch and Instruction Decode
- Exec: ALU operates on the two register operands
- Wr: Write the ALU output back to the register file




Structural Hazard

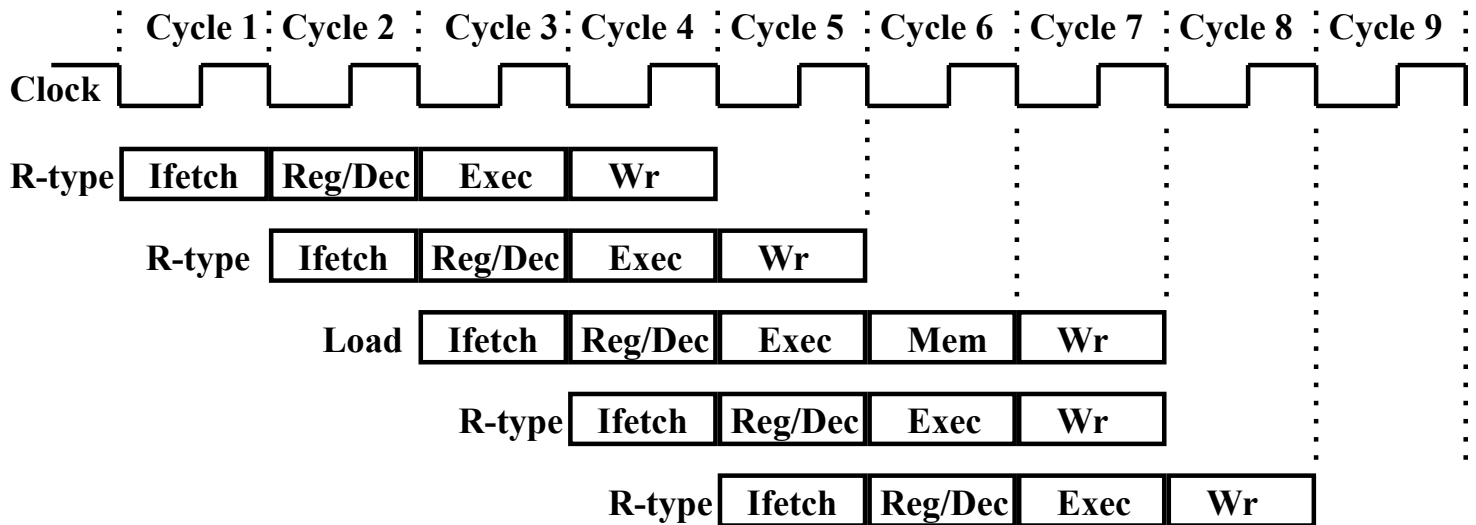- Interaction between R-type and loads causes structural hazard on writeback



Structural Hazard

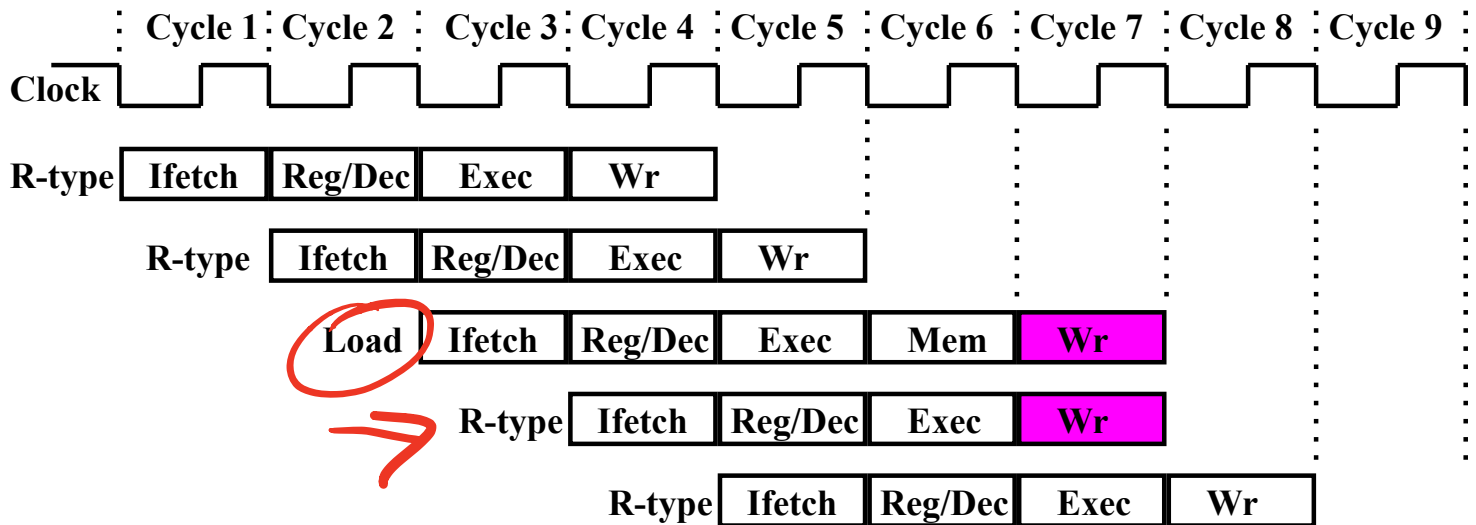- Interaction between R-type and loads causes structural hazard on writeback



Structural Hazard: Solved

- Add a do-nothing (NO OP or NOP) MEM stage

