


0x04 - Flops and Metrics

ENGR 3410: Computer Architecture


Jon Tse

Fall 2020


Feedback - Workload

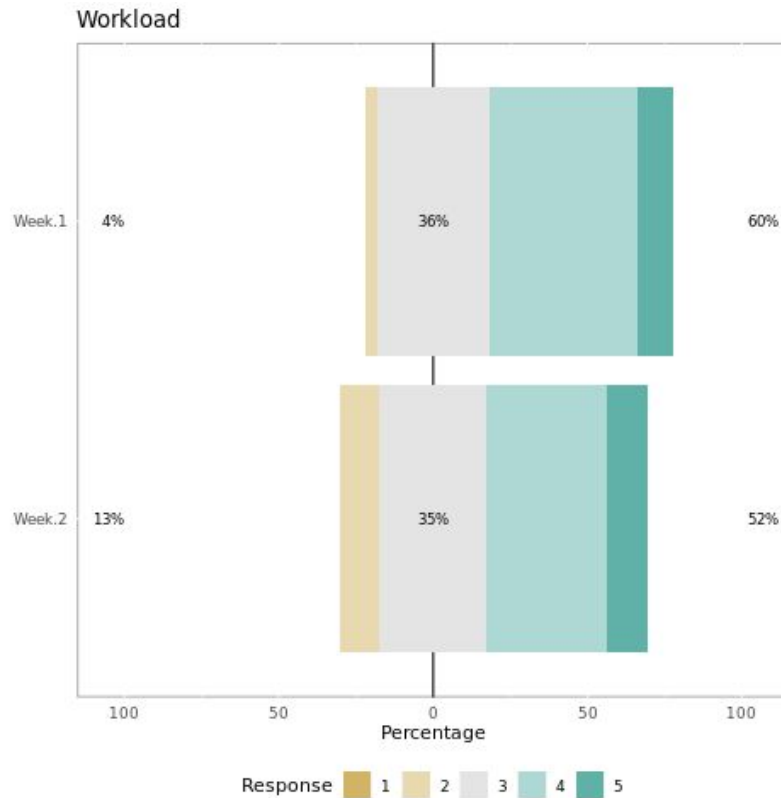

Feedback - Pace

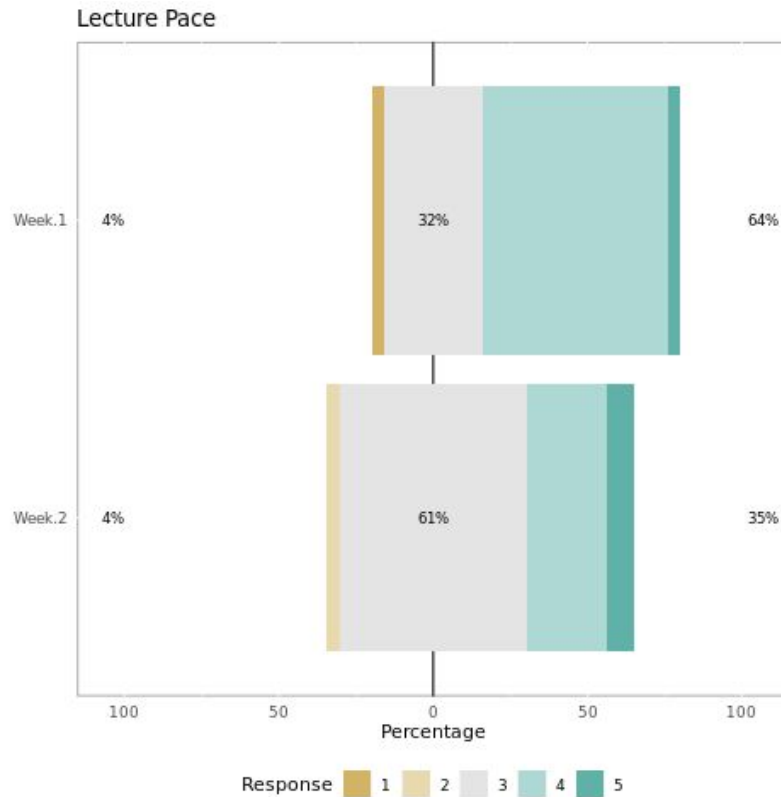


Feedback - Understanding

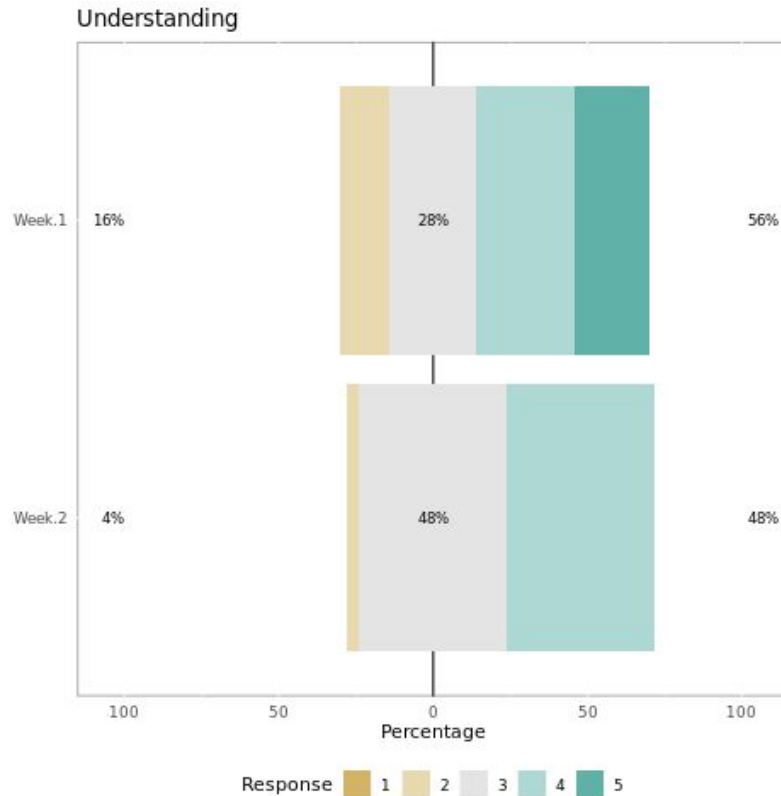

Feedback - Unix

Verilog/UNIX/Docker Comfort Level


23 responses

 

Feedback - More Time On?

I wish we spent more time on...

23 responses

 

Feedback - Communication

Justified Expressions of Frustration

- I'm having issues with the lab.
- I have been debugging and can't figure it out.
- I'm stuck!

Actionable Requests for Help


- My full and half adder are working, but my ripple carry adder testbench reports failures. I don't understand why!
- iverilog gives me <X> error message!?

Feedback - Final Project


Scheduling Question

Lab Discussion


Review

 


\bar{S}	\bar{R}	Q
0	0	:(
0	1	1
1	0	0
1	1	Q

 


Review

 


\overline{S}	\overline{R}	Q
0	0	:(
0	1	1
1	0	0
1	1	Q

 

 


Review

 

S	R	E	Q_{next}
0	0	1	Q_{curr}
0	1	1	0
1	0	1	1
1	1	1	:(
X	X	0	Q_{curr}

Handwritten table with red ink:

NAND		
A	B	Q
0	1	1
1	0	1
1	1	0

 

D	E	Q_{next}
0	0	Q_{curr}
1	0	Q_{curr}
0	1	0
1	1	1

Today


Finish up State Holding Elements

Look at Examples of Design Metrics

How to evaluate said metrics


Digestible examples, not memorization fodder

Data "D" Latch

 

D	E	Q_{next}
0	0	Q_{curr}
1	0	Q_{curr}
0	1	0
1	1	1



D	E	\bar{S}	\bar{R}
X	0	1	1
0	1	1	0
1	1	0	1

 

$g(f(x))$


Data "D" Flip Flop

  Two D-Latches in Series
Opposite Enable Polarity



Edge Triggered D-Flip Flop

 - Functionally similar to prior dual latch flip flop
- Edge Triggered, not Pulse
- Implementation process dependent
 - Can be roughly three SR Latches
 - Can be dynamic logic – learn in VLSI





Edge Triggered D-Flip Flop *edge*

- Always has:

- Clk, D, Q

Rising edge

Clk	D	Q
↑	0	0
↑	1	1
Other	X	Q

  


Edge Triggered D-Flip Flop

- Always has:

- Clk, D, Q

Clk	D	Q
↑	0	0
↑	1	1
Other	X	Q

 

- May also have:

- S, R, $\sim Q$

- **S**et and **R**eset are asynchronous (ignore clock)

- Can be used to define initial conditions (e.g. at boot)


Reminder

Lots of different Flop/Latch types

Each type has little idiosyncrasies

Big Picture - Hold State, Time Matters

Can be clocked or enabled

 

Common Uses

- In between processing stages
- “Debounce” inputs
 - Hide external noise / uncertainty from the inputs
- Synchronization

Design Evaluation

Area

Delay/Performance

Energy/Power - Next Time

≡ Do ≠ Do ≡ Do


Full Adder

Calculate Propagation Delays


Multiple Paths? Choose Worst

	A	B	Cin
Sum	6	6	3
Cout	5	5	2

A	B	CI	CO	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Multi-Bit Addition

 


Using previous slides' design, find worst prop delay

	A	B	Cin
Sum	6	6	3
Cout	5	5	2

	A/B0	A/B1	A/B2
S0	6	—	—
C1	5	—	—
S1	5+3	6	—
C2	5+2	5	—
S2	5+2+3	5+3	6
C3	5+2+2	5+2	5

Multi-Bit Addition

 

Using previous slides' design, find worst prop delay


	A	B	Cin
Sum	6	6	3
Cout	5	5	2

	A/B0	A/B1	A/B2
S0	6	-	-
C1	5	-	-
S1	5+3	6	-
C2	5+2	5	-
S2	5+2+3	5+3	6
C3	5+2+2	5+2	5

Full Adder as a LUT in Gates


- Only half, slide too small to show Sum

- Area Cost?



 


- Speed?


	A	B	Cin
Sum	3	3	3
Cout	3	3	3

 


NAND-2

   

NAND-4

 

Timing with Alternate Topology

 

Using new prop delays,
find total delay

	A	B	Cin
Sum	3	3	3
Cout	3	3	3

	A/B0	A/B1	A/B2
S0	3	-	-
C1	3	-	-
S1	3+3	3	-
C2	3+3	3	-
S2	3+3+3	3+3	3
C3	3+3+3	3+3	3

Growth Rates

- What changes as a specific design 'grows'
 - Propagation delay
 - Silicon area
- Propagation Delay for an N bit adder?
 - Design 1: NAND Gates
 - Design 2: Small LUT


Growth Rates

- What changes as a specific design 'grows'
 - Propagation delay
 - Silicon area
- ~~Propagation Delay~~ for an N bit adder?
 - Design 1: $2N + 5$
 - Design 2: $3N$
- Which design is faster? Larger?

Size in Silicon

- Physical Area drives manufacturing cost
 - # Chips per silicon wafer

$\boxed{10} =$

 

- Number of inputs drives gate size
 - Two transistors per input
 - Slightly worse than linear growth
- Total Gate Inputs ☐ Rough Cost Estimate

$$S = \{s_1, s_0\}$$

Decoder Growth


s_1	s_0	0_0	0_1	0_2	0_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- For a decoder with **S** select bits and **D** outputs
 - $D = 2^S$


- Need
 - S** Inverters
 - D** AND Gates with **S** inputs $\rightarrow DS$

- Total Size:
 
$$DS + S = S(2^S + 1) = (D + 1) \log_2 D$$




Look Up Table w/Decoder

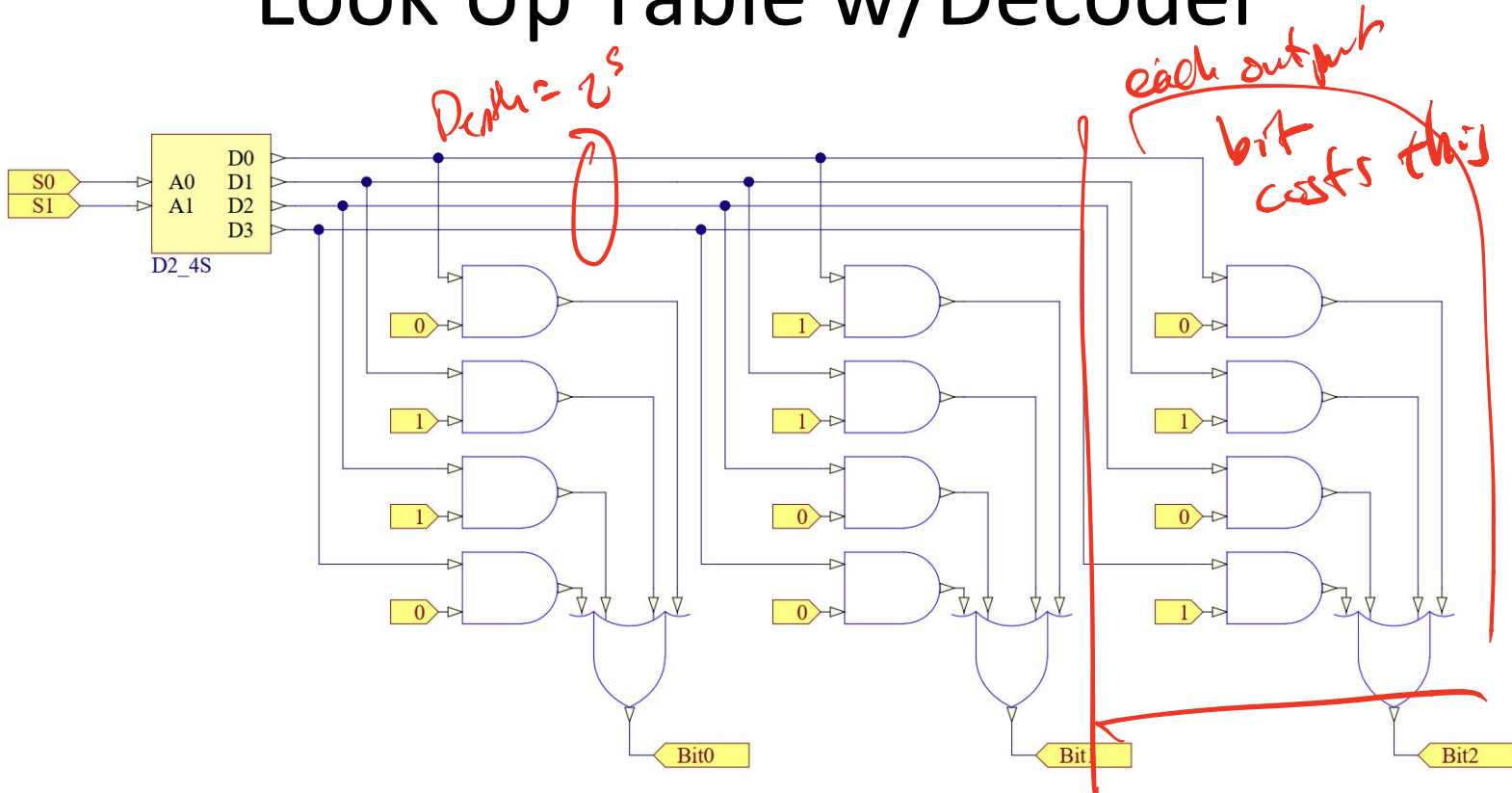

Growth Characteristics

 - This has 12 Gate Inputs
 - 4 AND2 (8)
 - 1 OR4 (4)
- Per decode line:
 - 1 AND2
 - 1 input of the OR
- $(\text{\#Decode Lines}) * 3$



LUT Growth Review


- For a LUT with Depth **D** and Output Width **W**
- Need
 - 1 Decoder
 - **W** Output Structures
- Total Size:

LUT Growth Review

- For a LUT with Depth **D** and Output Width **W**
- Need
 - 1 Decoder $(D+1)\log_2(D)$
 - **W** Output Structures $W(3D)$
- Total Size: $(D+1)\log_2(D) + W(3D)$

Single stage adder

 - Returning to our adder example, how does the size of each implementation scale?




Full Adder

Calculate Propagation Delays

Multiple Paths? Choose Worst

	A	B	Cin
Sum	6	6	3
Cout	5	5	2


A	B	CI	CO	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Full Adder as a LUT in Gates


- Only shows Cout, need another LUT for Sum
- How to build a LUT

	A	B	Cin
Sum	3	3	3
Cout	3	3	<u>3</u>

 

Single stage adder

 - Let's eliminate propagation delay by implementing an adder as large single LUT...



Adder Comparison

LUT for 32bit + 32bit = 32bit addition

- $S = (32+32) = 64$
- $W = 32$
- $D = 2^S = 18446744073709551616$

Total Size = $(D+1)\log_2(D) + W(3D)$

$2951479051793528258624 \approx 3 \times 10^{21}$

Adder Comparison

- LUT for 32bit + 32bit = 32bit addition
 - Size $\approx 3 * 10^{21}$
- Chained Full Adder
 - 9 NAND2 Gates per bit
 - Size = $32 * 18 = 576$
- Apollo Guidance Computer
 - 4100 NOR3

Better Gate Delay Estimation

- Model gate delay as proportional to the number of inputs in the gate
- Basic gates: NAND, NOR, NOT
- AND, OR, etc have “hidden” extra inverters
- e.g. for unit delay of 10:
 - 8-input NOR delay = 80
 - 8-input OR delay = 90 (extra inverter)