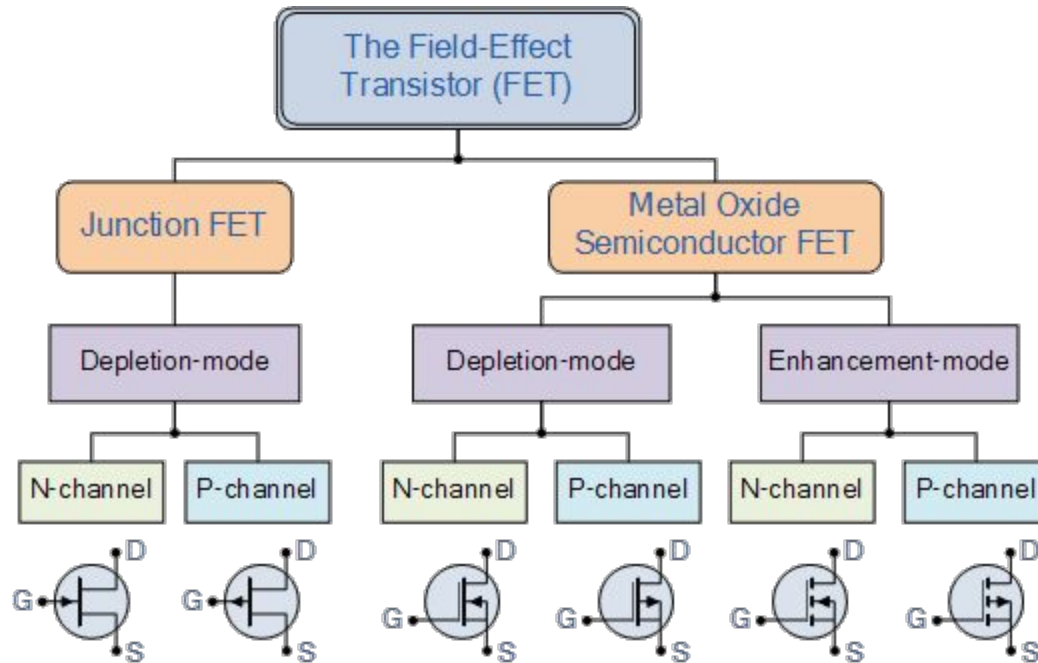


Gates in CMOS


CMOS

- CMOS stands for “complementary metal-oxide semiconductor”
- Used to construct:
 - digital circuitry
 - memory
 - some analog circuits




FETs



How they work

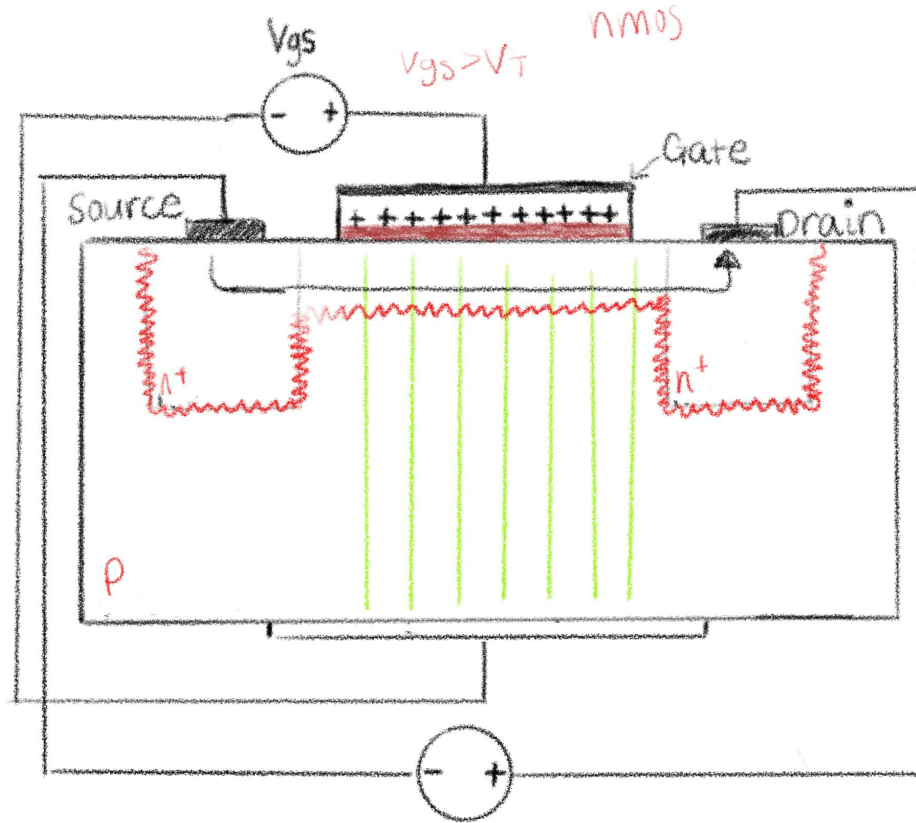


SR Model for MOSFET

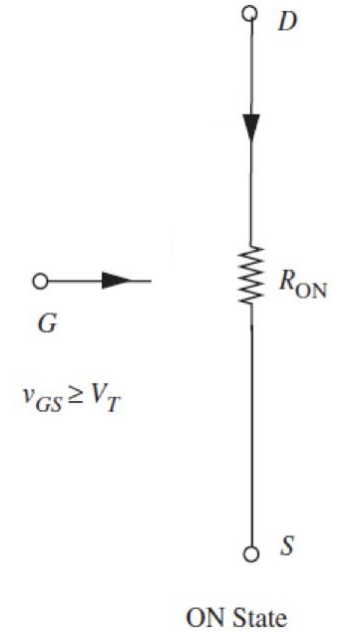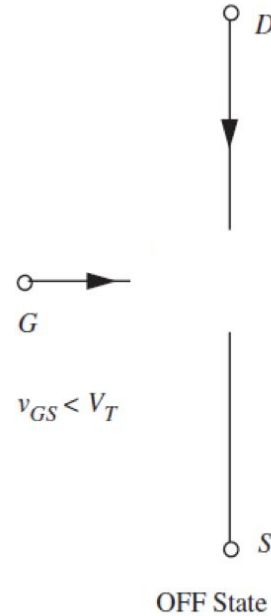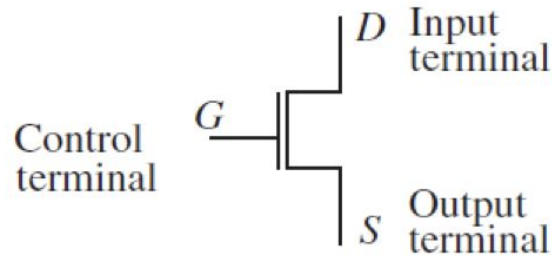


FinFET

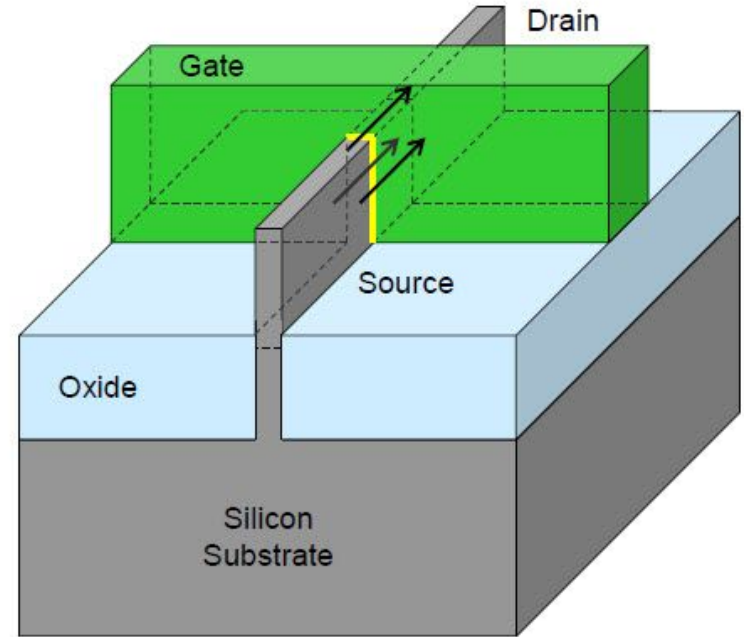- Has the same functions as MosFets
- When gate electrode is energized it has more control due to it surrounding the channel




MosFET vs FinFET

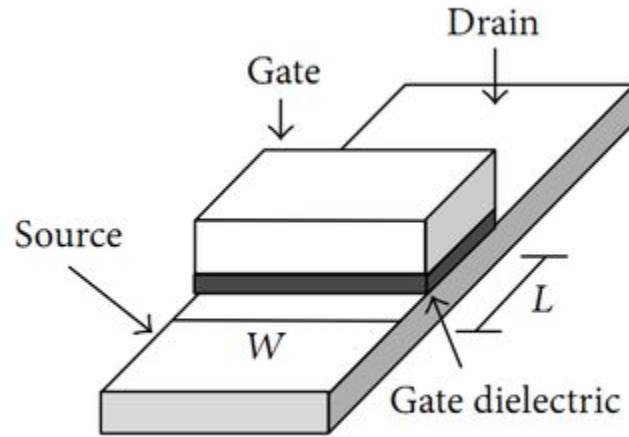

(a)

MosFET

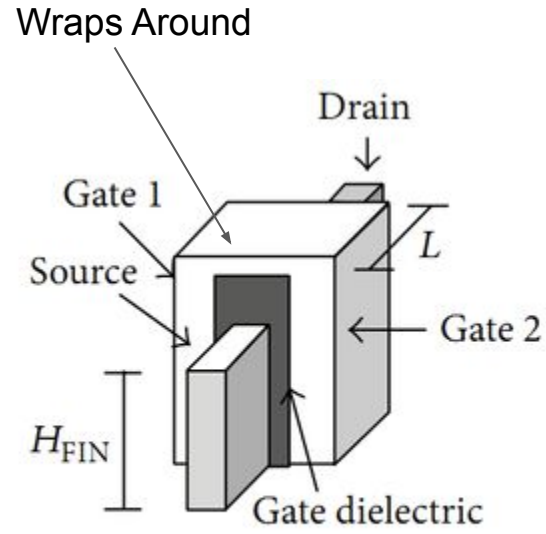

(b)


FinFET

NOT (Inverter)

A	Y
0	1
1	0


M1		
A	S	D
0	1	S
1	1	X

M2		
A	S	D
0	0	X
1	0	S

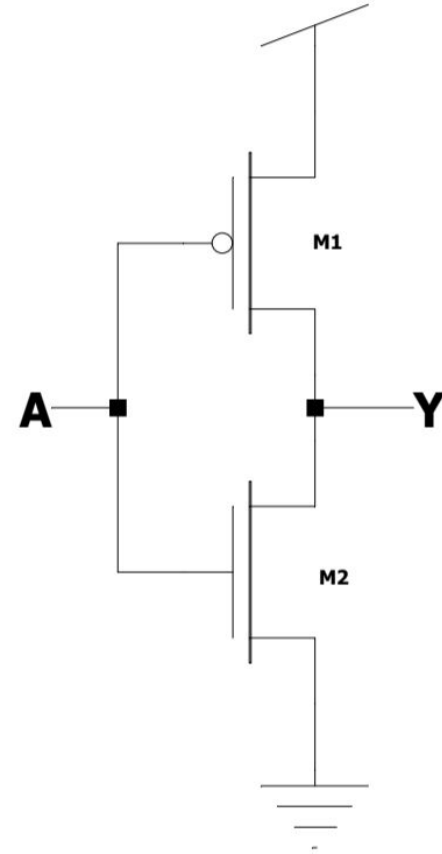


NAND

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

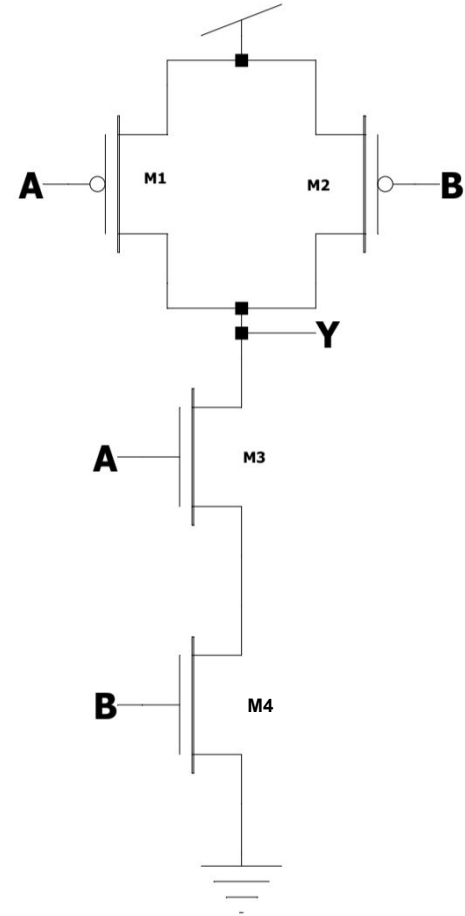

NOR

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

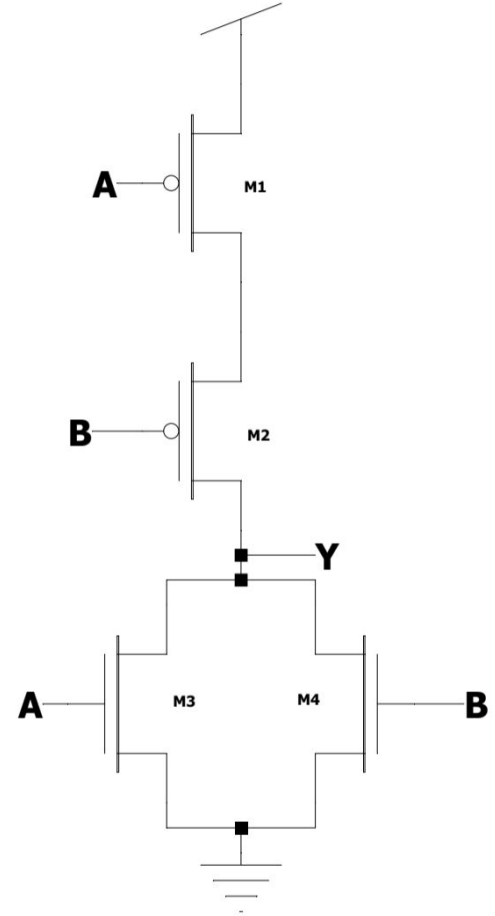

Pass-Transistor Logic -> Passgates


- Fewer devices
- Eliminates redundant transistors
- Lower switching energy

Drawbacks:

V_t loss -> static power consumption + slower transition


Passgate AND

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

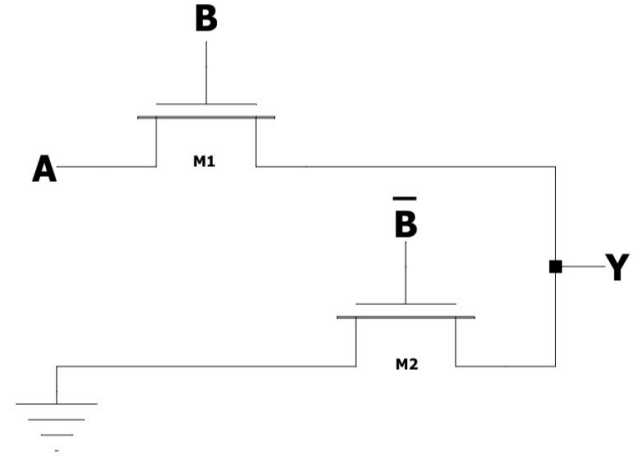


Passgate OR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

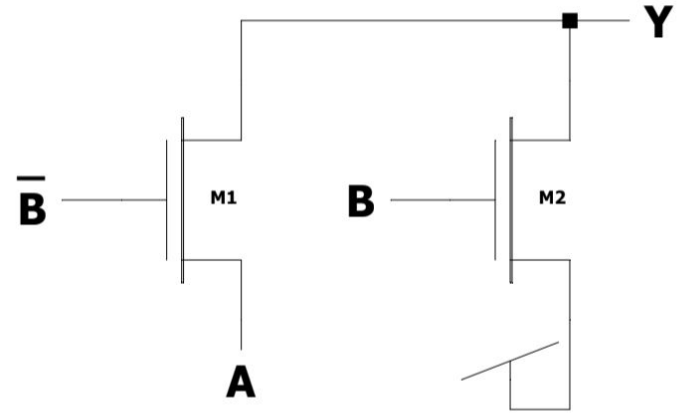

Passgate XOR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

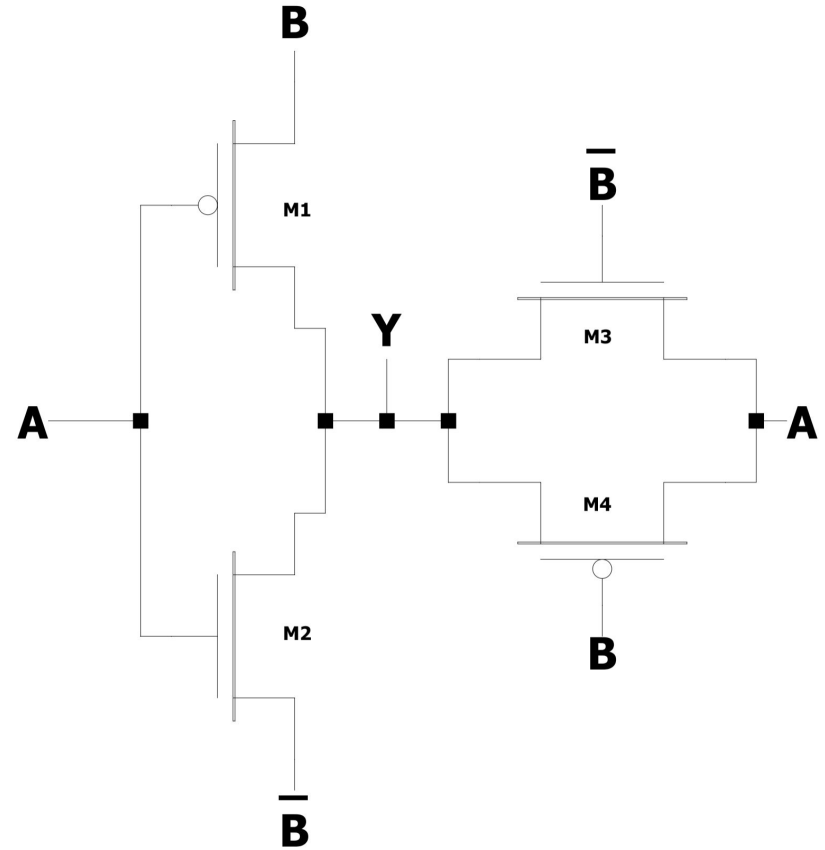

Questions?