


0x08 - Memory and Finite State Machines

ENGR 3410: Computer Architecture


Jon Tse

Fall 2020


Feedback - Workload

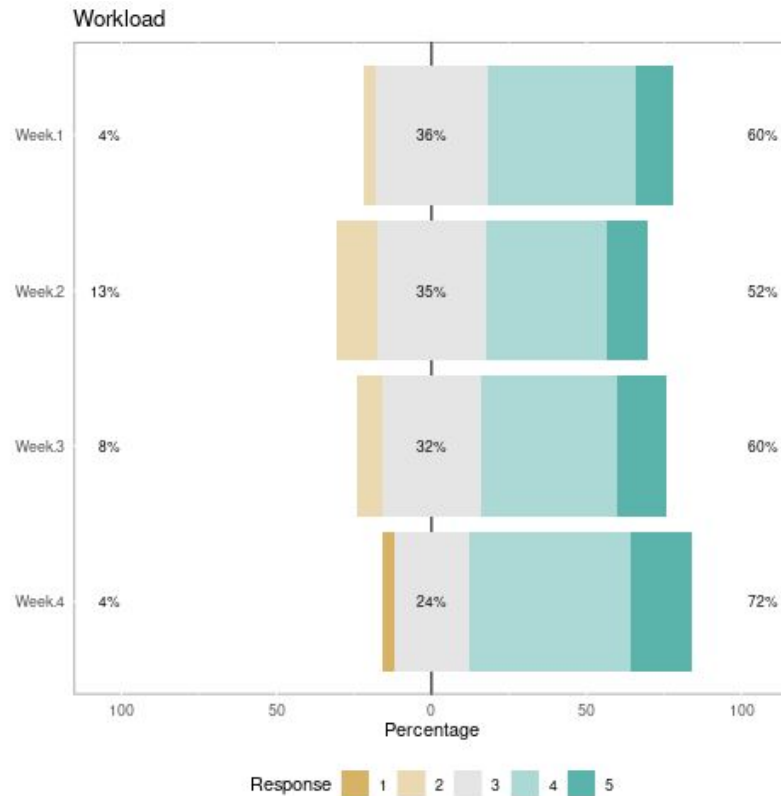


Feedback - Understanding

 

Feedback - Pace

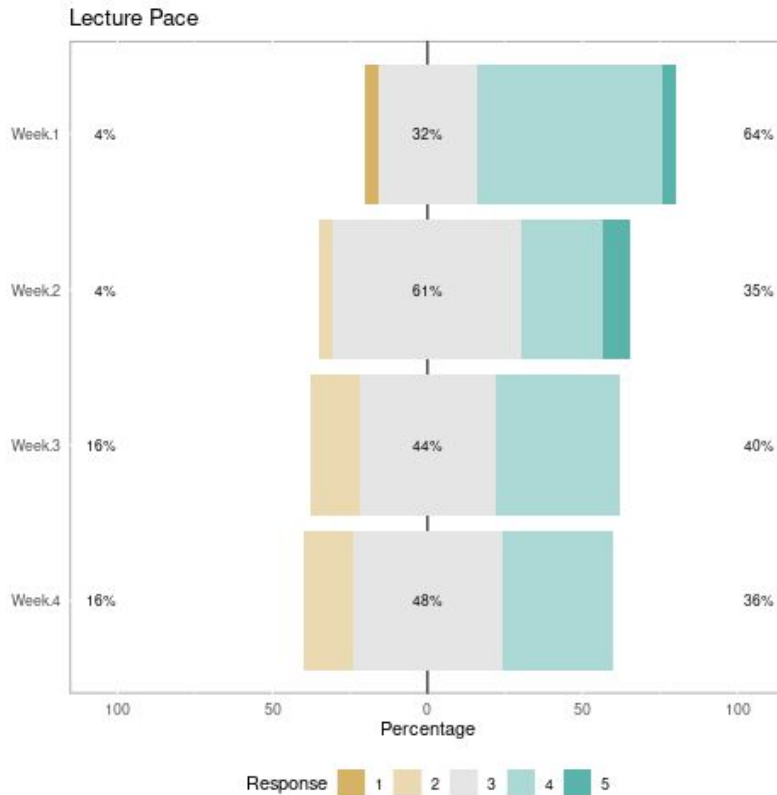


Feedback - Verilog

 

Feedback



I wish we spent more time on...

23 responses

 


Housekeeping

  - github - “master” branch -> “main” branch
- Discussion of HW5
- Discussion of Lab 2
- Discussion of Lab 3



Feedback

 - Delay in Verilog is confusing
- Issues with Makefiles
- You speed up when running out of time
- Class is getting more confusing...




Memory


Array Model

$w \text{ int } [w-1:0] \text{ MEM } [N-1:0]$

$\text{int}(W) \text{ MEM}[0..N-1]$

 


Enabled D-Flip Flop

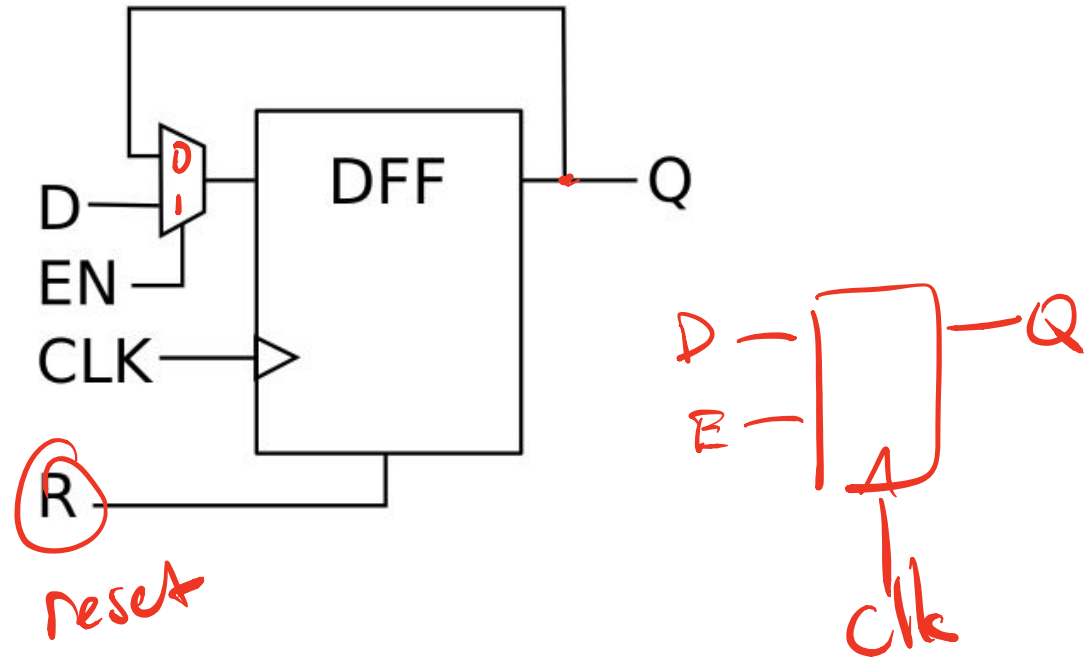


everything shares db


Implementing Register File

 

Implementing Register File

 

write enable

 


2-bit
2-word
register
file

read select

Implementing Register File

MEM[0]
MEM[15]
⋮
MEM[N]

 


Finite State Machines

Collection of States (Node) and Transitions (Edge)


Transitions are guarded by conditions.

Example: ~~Refrigerator~~ ^{Heater}

 

Finite State Machines

 
- In Computer Architecture, FSMs:
 - Usually transition on a clock edge
 - Are Complete
 - All states define transitions for all inputs
 - Are deterministic



FSM Implementation

State₂ 0
State₂ ϕ

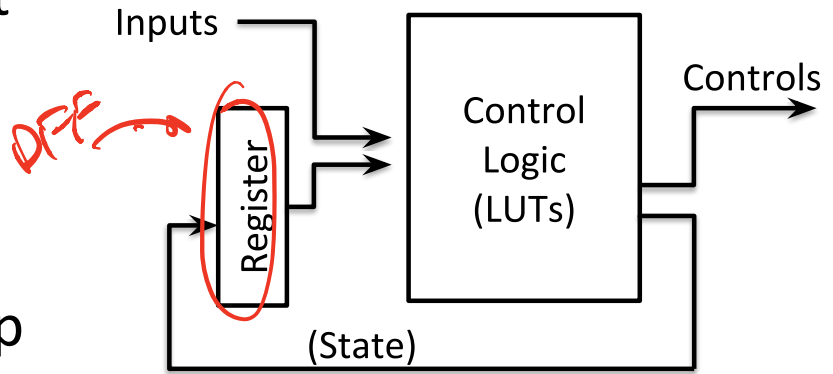
- Register to hold current state
- Wires to provide inputs (arguments)
- Look Up Table(s) to map transitions



Old		New
Current State	Inputs	Resulting State
Heater Off	Too Cold	Heater On
Heater Off	---	Heater Off
Heater On	Too Hot	Heater Off
Heater On	---	Heater On

Transitions -> LUT


Current State	Inputs	Resulting State
Heater Off	Too Cold	Heater On
Heater Off	---	Heater Off
Heater On	Too Hot	Heater Off
Heater On	---	Heater On

 

<i>input</i>		<i>output</i>	
State	Cold?	Hot?	Next State
Off	Yes	Yes	X
Off	Yes	No	On
Off	No	Yes	Off
Off	No	No	Off
On	Yes	Yes	X
On	Yes	No	On
On	No	Yes	Off
On	No	No	On

LUT -> Circuit


State	Cold?	Hot?	Next State
Off	Yes	Yes	X
Off	Yes	No	On
Off	No	Yes	Off
Off	No	No	Off
On	Yes	Yes	X
On	Yes	No	On
On	No	Yes	Off
On	No	No	On

 

$$q_{NEXT} = (Cold) + (\overline{Hot})q$$

FSM Process Summary

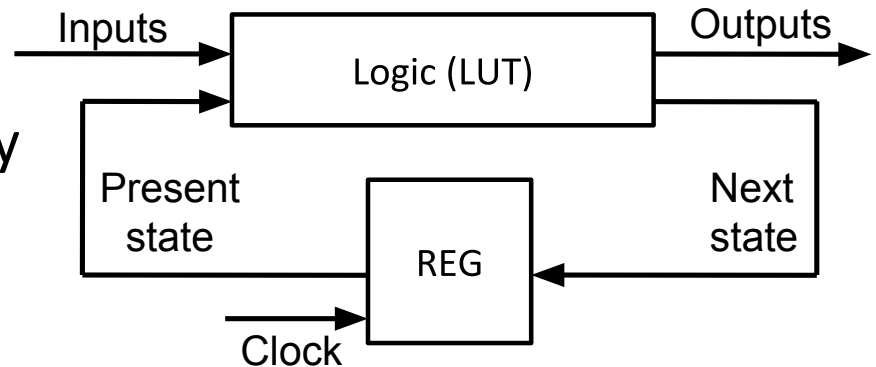- Design Requirements
- Define States
- Define Transitions
- Assign Values / Binary Codes
- Calculate Widths
- Make a LUT
- Connect Registers
- (Optional) Simplify



Binary Encoding

- States are stored as binary numbers
- Requires $\lceil \log_2 N \rceil$ registers for N states
- LUT requires a decoder (per usual)

One Hot Encoding

- States are stored as one bit being “hot”
- Requires N registers for N states
- LUT doesn't require a decoder


Binary	One Hot
00	0001
01	0010
10	0100
11	1000

One Hot Construction

- LUT Method works:
 - N states = N LUT address bits (+ input bits)
 - This creates many “don’t care” LUT rows
 - 2^N rows, only care about N of them
- LUT Simplification
 - Same process as before
 - Apply LOTS of simplification



One Hot Construction

 - Start with Flow Diagram
- Replace each state with a D Flip Flop
- D input is an OR gate
 - Each input is a transition



One Hot Construction

  - Start with Flow Diagram
- Replace each state with a D Flip Flop
- D input is an OR gate
 - Each input is a transition
 - Source State AND transition condition



Encoding Comparison

Binary

- Fewer Flip Flops
- Slower
- Wider LUTs

One Hot

- More Flip Flops
- Faster Clock Speeds
- Simpler Logic
- Many Illegal States
 - What if 2 bits are hot?
 - LOTS of “Don’t Cares” in logic

Wait States

- Typical Data Flow:
 - FSM creates control signals for a clocked element
 - Other element takes N cycles to finish
 - FSM proceeds to next task
- Wait States delay the FSM
 - Very Simple ☐ Single Transition
 - One Hot ☐ Just a D Flip Flop, no logic!

